

# ELECTRICAL ANALOGY

## Objectives

- To draw electrical analogous circuits (loop and nodal circuits) for the given mechanical system (translational and rotational)
- To derive the dynamic equations for mechanical systems as well as the analogous electrical circuits and show one to one analogous equivalence between them and thus verifying the analogy.

## Why is this electrical analogy important ?

- Mechanical, thermal, hydraulic and electromechanical systems could be represented and studied by their equivalent electrical circuits which are most easily constructed than the corresponding models.
- The equations of electrical and the corresponding mechanical or hydraulic systems are compared and from that equivalent electrical circuits are obtained. If the differential equations of both electrical and mechanical or hydraulic systems are equal, then one system is said to be analogous to the other.

# FORCE VOLTAGE ANALOGY

**MECHANICAL SYSTEM:**

Input – force


Output – Velocity

**ELECTRICAL SYSTEM:**

Input – Voltage source

Output – current through the element


**Mass**

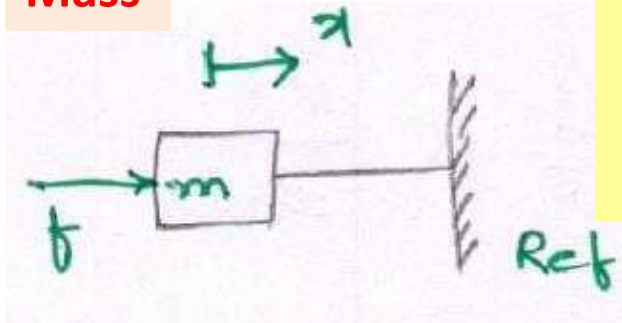

$$f(t) = M \frac{d^2 x}{dt^2}$$


$$= M \frac{dv}{dt}$$

**Dash pot**

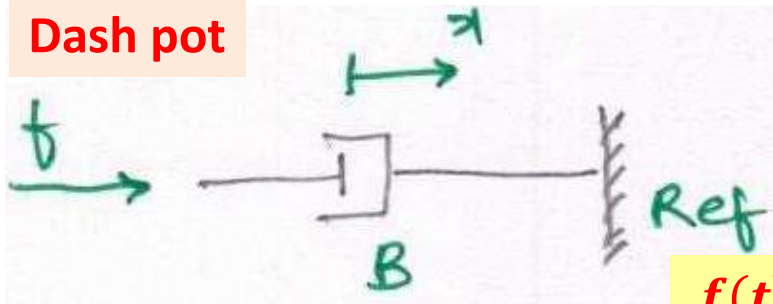

$$f(t) = Bv$$


**Spring**

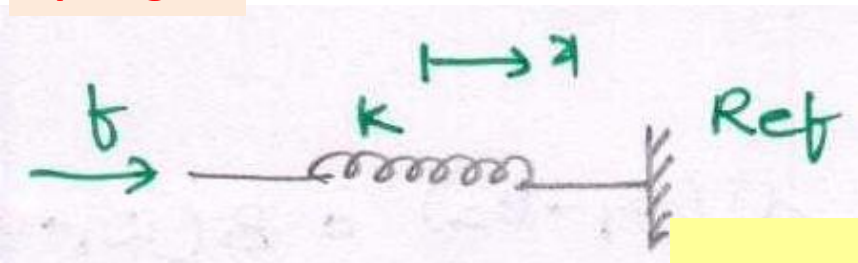

$$f(t) = Kx = K \int v dt$$


	$f(t)$	$e(t)$	
	$v$	$i$	
$M \frac{dv}{dt}$	$M$	$L$	$L \frac{di}{dt}$
$Bv$	$B$	$R$	$iR$
$K \int v dt$	$K$	$\frac{1}{C}$	$\frac{1}{C} \int i dt$

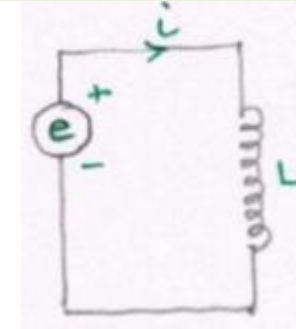$f(t)$  – Applied force  
 $B$  – Damping Coefficient  
 $K$  – Spring Stiffness




**Inductance**

$$e(t) = L \frac{di}{dt}$$

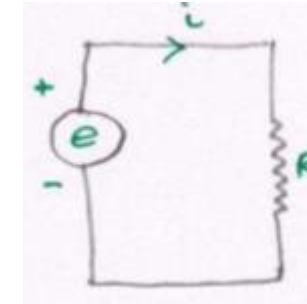

**Resistance**

$$e(t) = iR$$

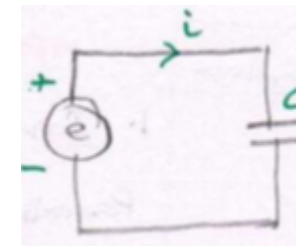

**Capacitance**

$$e(t) = \frac{1}{C} \int i dt$$

# FORCE VOLTAGE ANALOGY

## MECHANICAL SYSTEM

- Input – force
- Output – velocity

	Mechanical System	Electrical System	
	$f(t)$	$e(t)$	
	$v$	$i$	
$M \frac{dv}{dt}$	$M$	$L$	$L \frac{di}{dt}$
$Bv$	$B$	$R$	$iR$
$K \int v dt$	$K$	$\frac{1}{C}$	$\frac{1}{C} \int i dt$

## ELECTRICAL SYSTEM

- Input – voltage source
- Output – Current through the element

- In mechanical systems, elements having same velocity are said to be in series. Similarly, in electrical systems, the elements having same current are said to be in series.
- Each mass in the mechanical system corresponds to a closed loop in electrical system.
- Number of meshes in the electrical system is equal to the number of masses in the mechanical system
- The element connected between two masses in mechanical system is represented by common element between two meshes in electrical system.

# FORCE VOLTAGE ANALOGY

## MECHANICAL SYSTEM


- Input – force
- Output – velocity

	$f(t)$	$e(t)$	
	$v$	$i$	
$M \frac{dv}{dt}$	$M$	$L$	$L \frac{di}{dt}$
$Bv$	$B$	$R$	$iR$
$K \int v dt$	$K$	$\frac{1}{C}$	$\frac{1}{C} \int i dt$


## ELECTRICAL SYSTEM

Input – voltage source  
Output – Current through the element

## Mechanical System

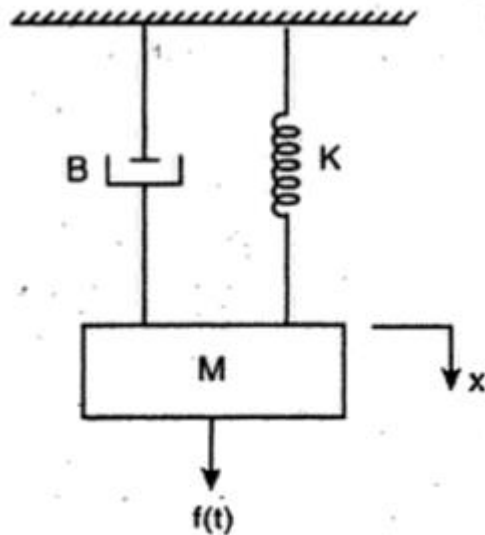

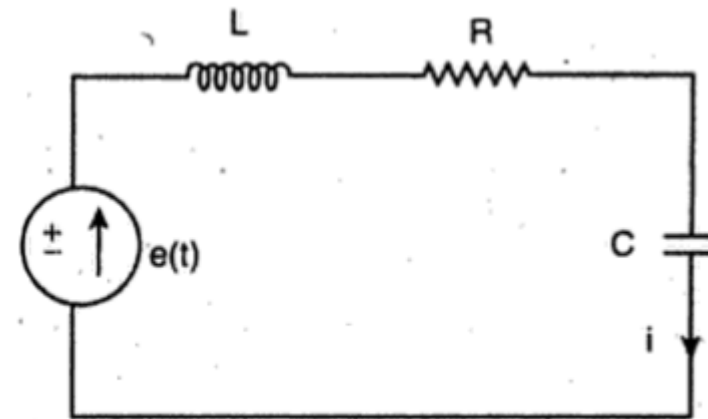
## Force Voltage Analogous Electrical circuit



# FORCE VOLTAGE ANALOGY

## MECHANICAL SYSTEM

- Input – force
- Output – velocity

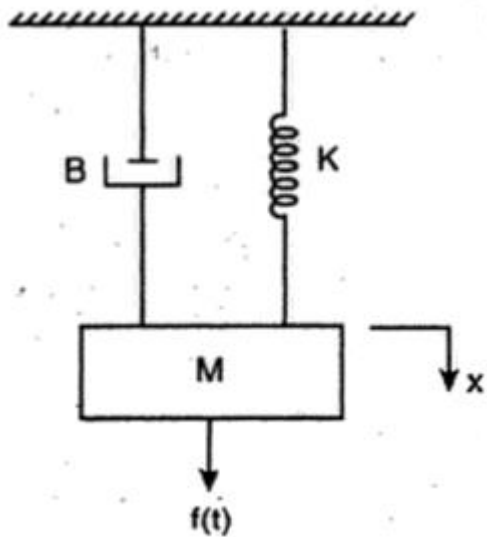

$$M \frac{d^2 x}{dt^2} + B \frac{dx}{dt} + Kx = f(t)$$

$$M \frac{dv}{dt} + Bv + K \int v dt = f(t)$$


	$f(t)$	$e(t)$	
	$v$	$i$	
$M \frac{dv}{dt}$	$M$	$L$	$L \frac{di}{dt}$
$Bv$	$B$	$R$	$iR$
$K \int v dt$	$K$	$\frac{1}{C}$	$\frac{1}{C} \int i dt$

## ELECTRICAL SYSTEM

Input – voltage source


Output–Current though the element

Force Voltage Analogous circuit

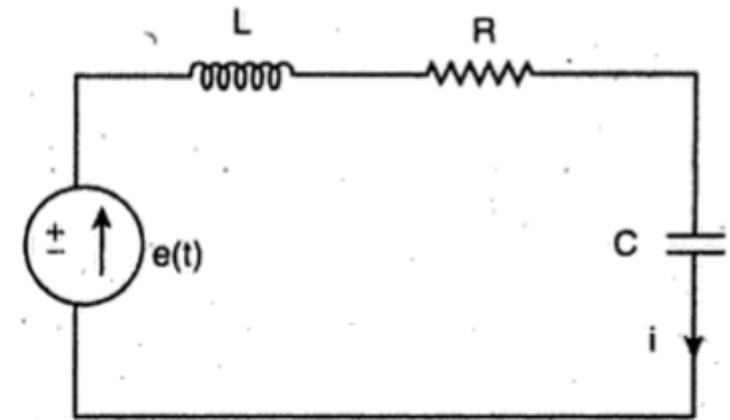

$$L \frac{di}{dt} + iR + \frac{1}{C} \int i dt = e(t)$$

# FORCE VOLTAGE ANALOGY

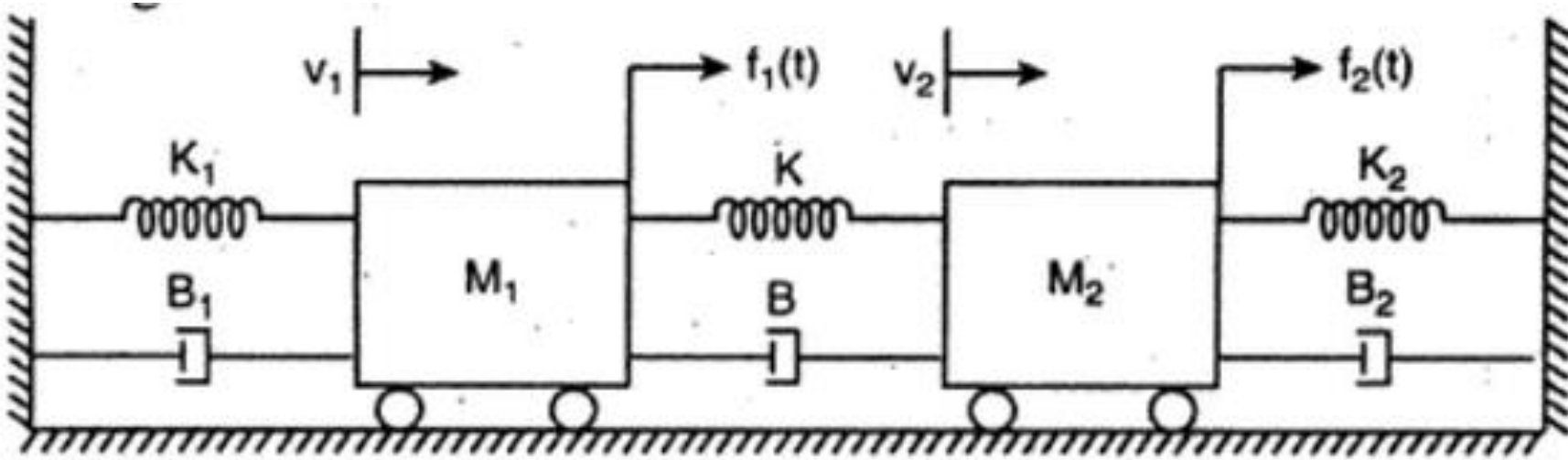


	$f(t)$	$e(t)$	
	$v$	$i$	
$M \frac{dv}{dt}$	$M$	$L$	$L \frac{di}{dt}$
$Bv$	$B$	$R$	$iR$
$K \int v dt$	$K$	$\frac{1}{C}$	$\frac{1}{C} \int i dt$

$$M_1 \frac{dv_1}{dt} + B_1 v_1 + K_1 \int v_1 dt + B(v_1 - v_2) + K \int (v_1 - v_2) dt = f_1(t)$$

$$M_2 \frac{dv_2}{dt} + B_2 v_2 + K_2 \int v_2 dt + B(v_2 - v_1) + K \int (v_2 - v_1) dt = f_2(t)$$

# FORCE VOLTAGE ANALOGY

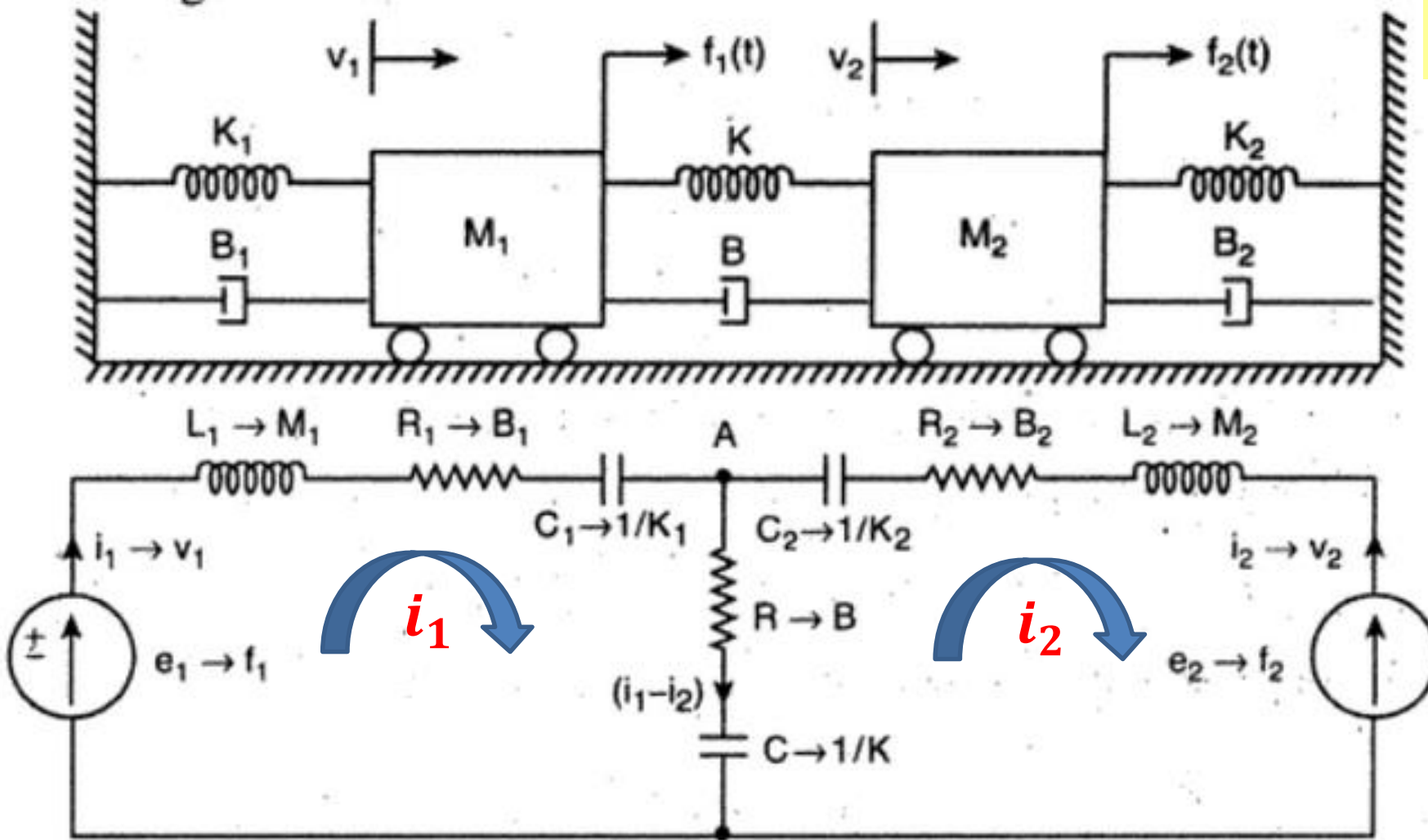

	$f(t)$	$e(t)$	
	$v$	$i$	
$M \frac{dv}{dt}$	$M$	$L$	$L \frac{di}{dt}$
$Bv$	$B$	$R$	$iR$
$K \int v dt$	$K$	$\frac{1}{C}$	$\frac{1}{C} \int i dt$

$$L_1 \frac{di_1}{dt} + i_1 R_1 + \frac{1}{C_1} \int i_1 dt + R(i_1 - i_2) + \frac{1}{C} \int (i_1 - i_2) dt = e_1(t)$$

$$L_2 \frac{di_2}{dt} + i_2 R_2 + \frac{1}{C_2} \int i_2 dt + R(i_2 - i_1) + \frac{1}{C} \int (i_2 - i_1) dt = e_2(t)$$




# FORCE CURRENT ANALOGY

**MECHANICAL SYSTEM:**      Input – force  
Output – Velocity

**ELECTRICAL SYSTEM:**


- Input – Current source
- Output – Voltage across the element

## Mass

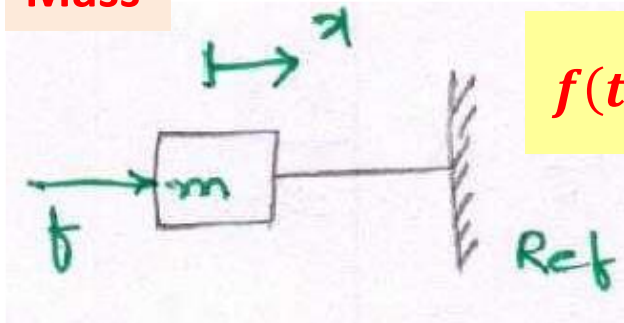


$$f(t) = M \frac{dv}{dt}$$

## Dash pot

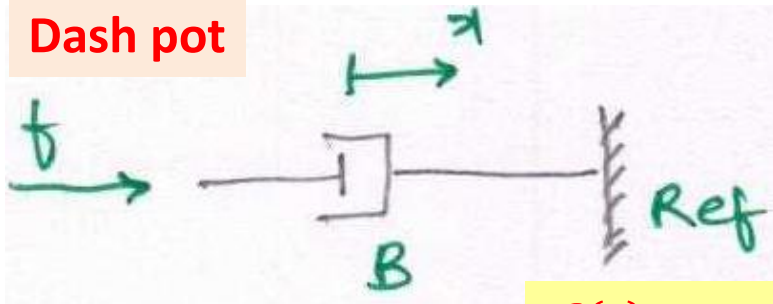

$$f(t) = Bv$$


## Spring

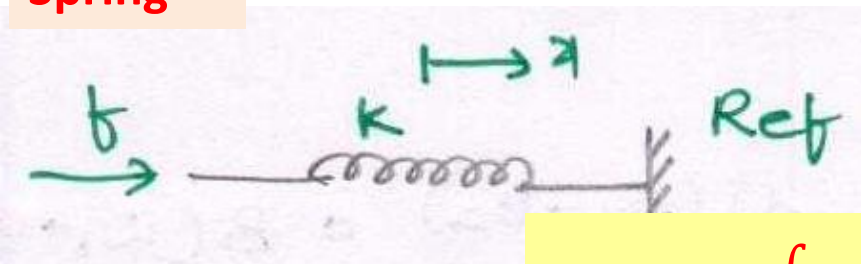

$$f(t) = K \int v dt$$


**$f(t)$  – Applied force**  
 **$B$  – Damping Coefficient**  
 **$K$  – Spring Stiffness**

## Capacitance

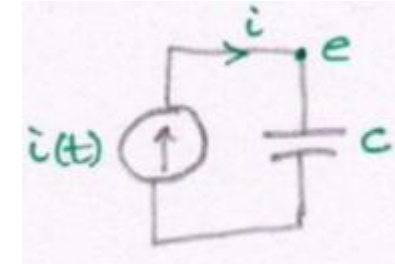


$$i(t) = C \frac{de}{dt}$$

## Resistance

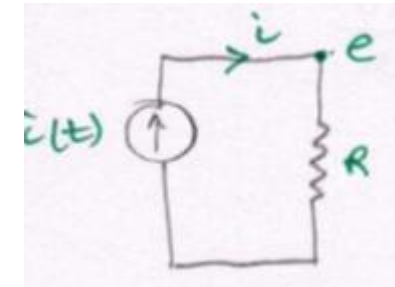

$$i(t) = \frac{e}{R}$$

## Inductance

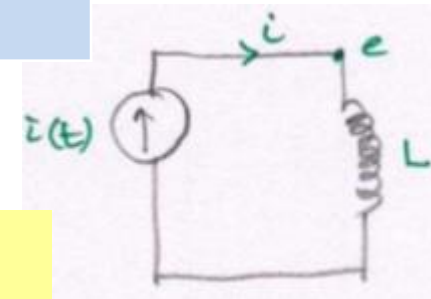

$$i(t) = \frac{1}{L} \int e dt$$



# FORCE CURRENT ANALOGY

## MECHANICAL SYSTEM

- Input – force
- Output – velocity

	Mechanical System	Electrical System	
	$f(t)$	$i(t)$	
	$v$	$e$	
$M \frac{dv}{dt}$	$M$	$C$	$C \frac{de}{dt}$
$Bv$	$B$	$\frac{1}{R}$	$\frac{e}{R}$
$K \int v dt$	$K$	$\frac{1}{L}$	$\frac{1}{L} \int e dt$

## ELECTRICAL SYSTEM


Input – current source  
Output – voltage across the element

- In mechanical systems, elements in parallel have same force. Similarly, in electrical systems, parallel systems will have same voltage.
- Each mass in the mechanical system corresponds to a node in a electrical system.
- Number of nodes in the electrical system is equal to the number of masses in the mechanical system
- The element connected between two masses in mechanical system is represented by common element between two nodes in electrical system.

# FORCE CURRENT ANALOGY

## MECHANICAL SYSTEM

- Input – force
- Output – velocity

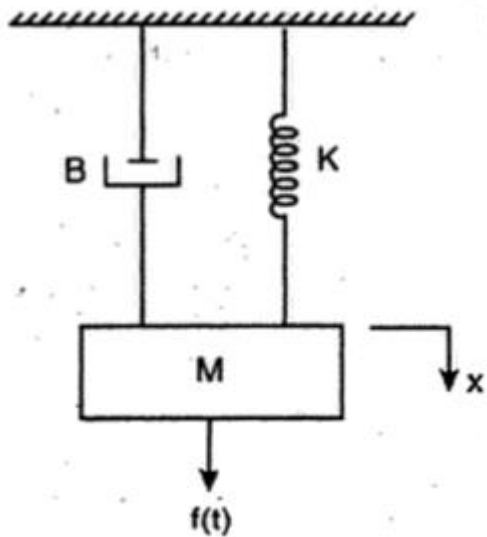

	$f(t)$	$i(t)$	
	$v$	$e$	
$M \frac{dv}{dt}$	$M$	$C$	$C \frac{de}{dt}$
$Bv$	$B$	$\frac{1}{R}$	$\frac{e}{R}$
$K \int v dt$	$K$	$\frac{1}{L}$	$\frac{1}{L} \int e dt$

$$M \frac{d^2 x}{dt^2} + B \frac{dx}{dt} + Kx = f(t)$$


$$M \frac{dv}{dt} + Bv + K \int v dt = f(t)$$

## ELECTRICAL SYSTEM

Input – voltage source


Output – Current through the element

Force Current Analogous circuit

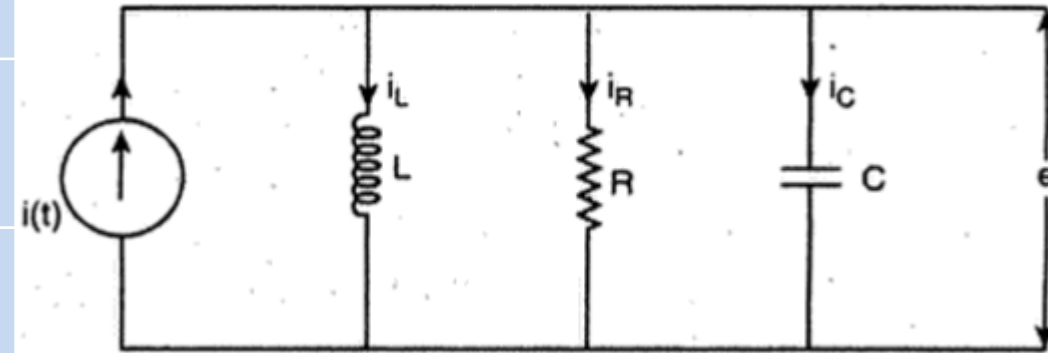

$$C \frac{de}{dt} + \frac{e}{R} + \frac{1}{L} \int e dt = i(t)$$



# FORCE CURRENT ANALOGY

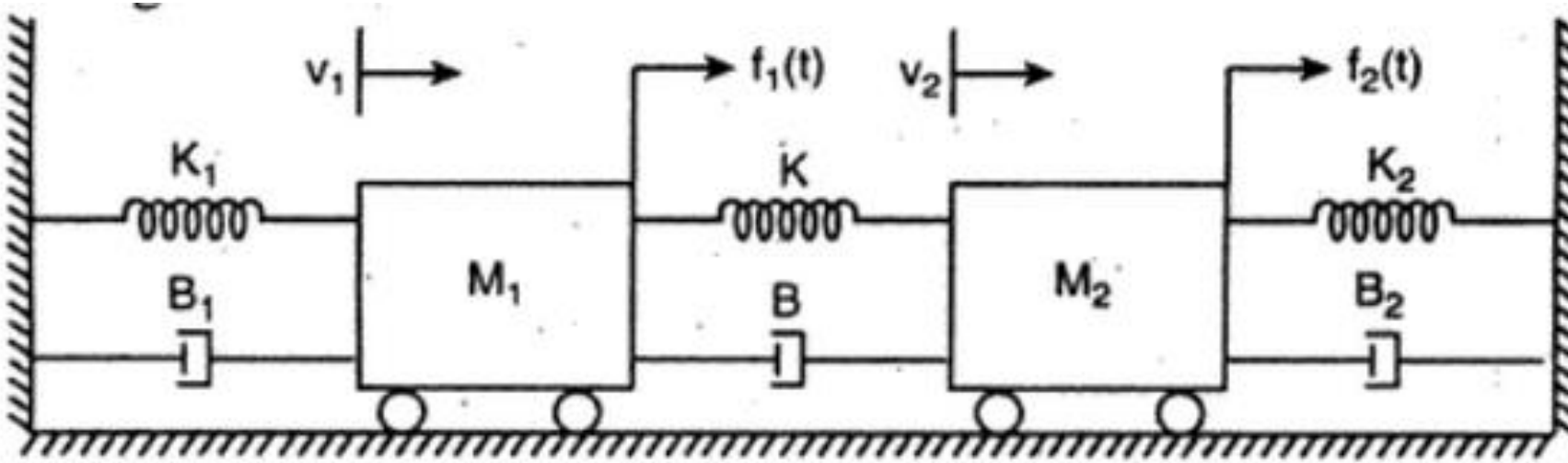

	$f(t)$	$i(t)$	
	$v$	$e$	
$M \frac{dv}{dt}$	$M$	$C$	$C \frac{de}{dt}$
$Bv$	$B$	$\frac{1}{R}$	$\frac{e}{R}$
$K \int v dt$	$K$	$\frac{1}{L}$	$\frac{1}{L} \int e dt$

$$M_1 \frac{dv_1}{dt} + B_1 v_1 + K_1 \int v_1 dt + B_1(v_1 - v_2) + K \int (v_1 - v_2) dt = f_1(t)$$
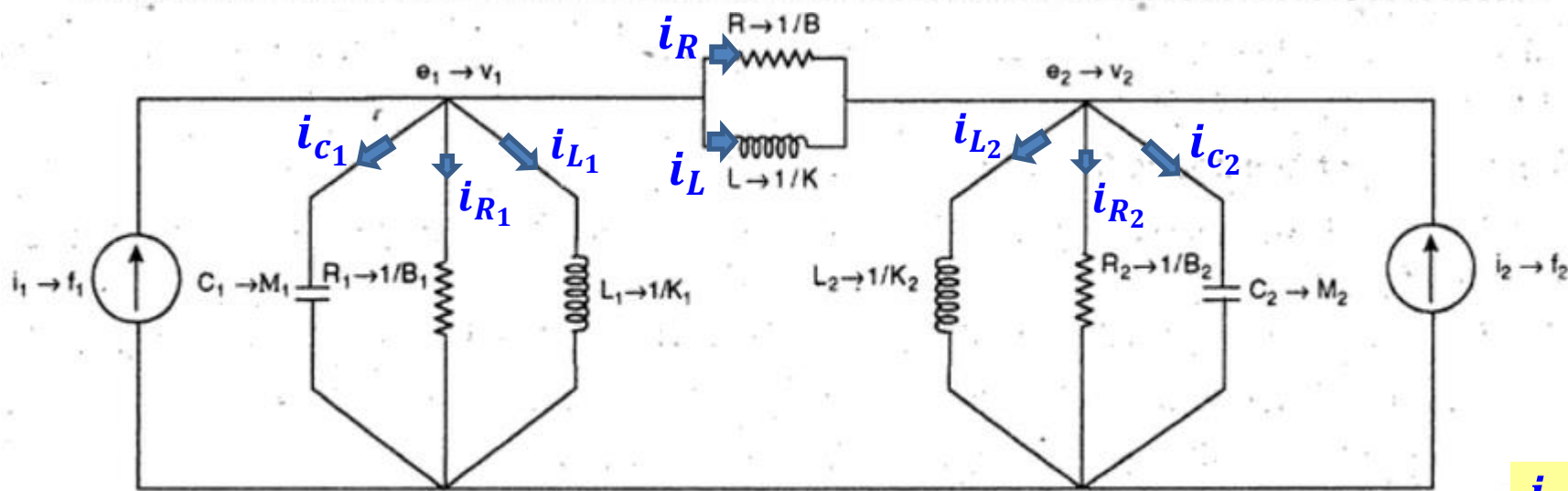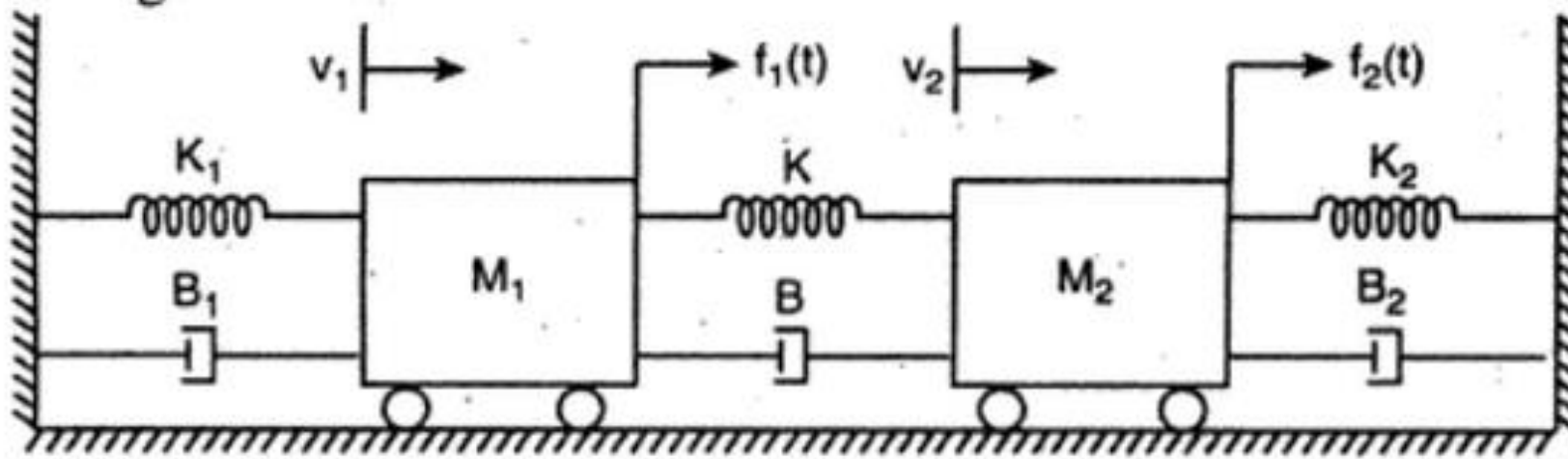
$$M_2 \frac{dv_2}{dt} + B_2 v_2 + K_2 \int v_2 dt + B(v_2 - v_1) + K \int (v_2 - v_1) dt = f_2(t)$$



	$f(t)$	$i(t)$	
	$v$	$e$	
$M \frac{dv}{dt}$	$M$	$C$	$C \frac{de}{dt}$
$Bv$	$B$	$\frac{1}{R}$	$\frac{e}{R}$
$K \int v dt$	$K$	$\frac{1}{L}$	$\frac{1}{L} \int e dt$

$$i_{c1} + i_{R1} + i_{L1} + i_R + i_L = i_1(t)$$

$$i_{c2} + i_{R2} + i_{L2} = i_2(t) + i_R + i_L$$

$$C_1 \frac{de_1}{dt} + \frac{e_1}{R_1} + \frac{1}{L_1} \int e_1 dt + \frac{e_1 - e_2}{R} + \frac{1}{L} \int (e_1 - e_2) dt = i_1(t)$$

$$C_2 \frac{de_2}{dt} + \frac{e_2}{R_2} + \frac{1}{L_2} \int e_2 dt = i_2(t) + \frac{e_1 - e_2}{R} + \frac{1}{L} \int (e_1 - e_2) dt$$


$$C_2 \frac{de_2}{dt} + \frac{e_2}{R_2} + \frac{1}{L_2} \int e_2 dt + \frac{e_2 - e_1}{R_1} + \frac{1}{L} \int (e_2 - e_1) dt = i_2(t)$$

# TORQUE VOLTAGE ANALOGY

**MECHANICAL SYSTEM:**     Input – Torque  
                                         Output – Angular Velocity


**ELECTRICAL SYSTEM:**     Input – Voltage source  
                                         Output – current through the element

**Moment of inertia of Mass**

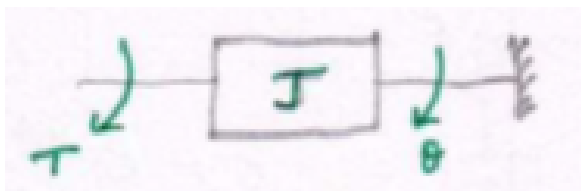


$$T(t) = J \frac{d^2\theta}{dt^2} = J \frac{d\omega}{dt}$$

**Dash pot**

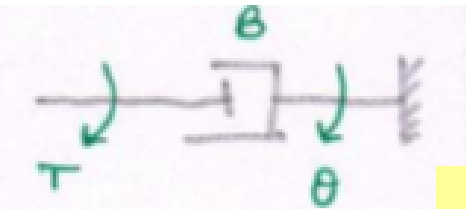

$$T(t) = B \frac{d\theta}{dt} = B\omega$$


**Spring**

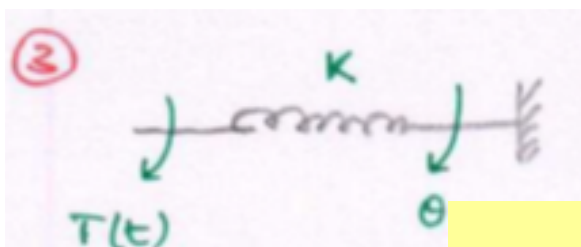

$$T(t) = K\theta = K \int \omega dt$$


	$T(t)$	$e(t)$	
	$\omega$	$i$	
$J \frac{d\omega}{dt}$	$J$	$L$	$L \frac{di}{dt}$
$B\omega$	$B$	$R$	$iR$
$K \int \omega dt$	$K$	$\frac{1}{C}$	$\frac{1}{C} \int i dt$

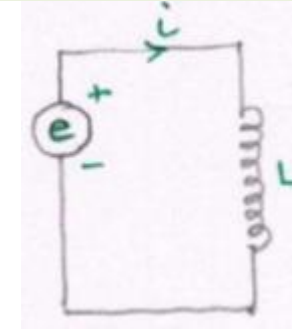$J$  – Polar Moment of Inertia  
 $\theta$  – Angular displacement  
 $\omega$  – Angular velocity




**Inductance**

$$e(t) = L \frac{di}{dt}$$

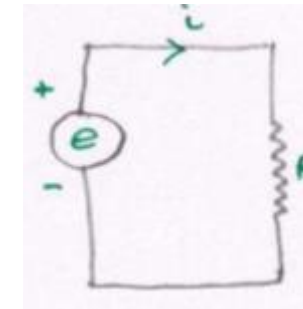

**Resistance**

$$e(t) = iR$$

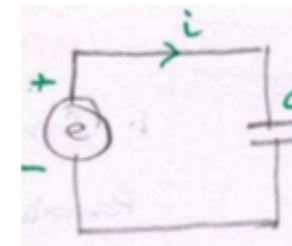

**Capacitance**

$$e(t) = \frac{1}{C} \int i dt$$

# TORQUE VOLTAGE ANALOGY

## MECHANICAL SYSTEM

- Input – Torque
- Output – Angular velocity


## ELECTRICAL SYSTEM

- Input – voltage source
- Output–Current though the element

	$T(t)$	$e(t)$	
	$\omega$	$i$	
$J \frac{d\omega}{dt}$	$J$	$L$	$L \frac{di}{dt}$
$B\omega$	$B$	$R$	$iR$
$K \int \omega dt$	$K$	$\frac{1}{C}$	$\frac{1}{C} \int i dt$

- In mechanical systems, elements having same angular velocity are said to be in series. Similarly, in electrical systems, the elements having same current are said to be in series.
- Each mass in the mechanical system corresponds to a closed loop in electrical system.
- Number of meshes in the electrical system is equal to the number of masses in the mechanical system
- The element connected between two masses in mechanical system is represented by common element between two meshes in electrical system.

# TORQUE VOLTAGE ANALOGY

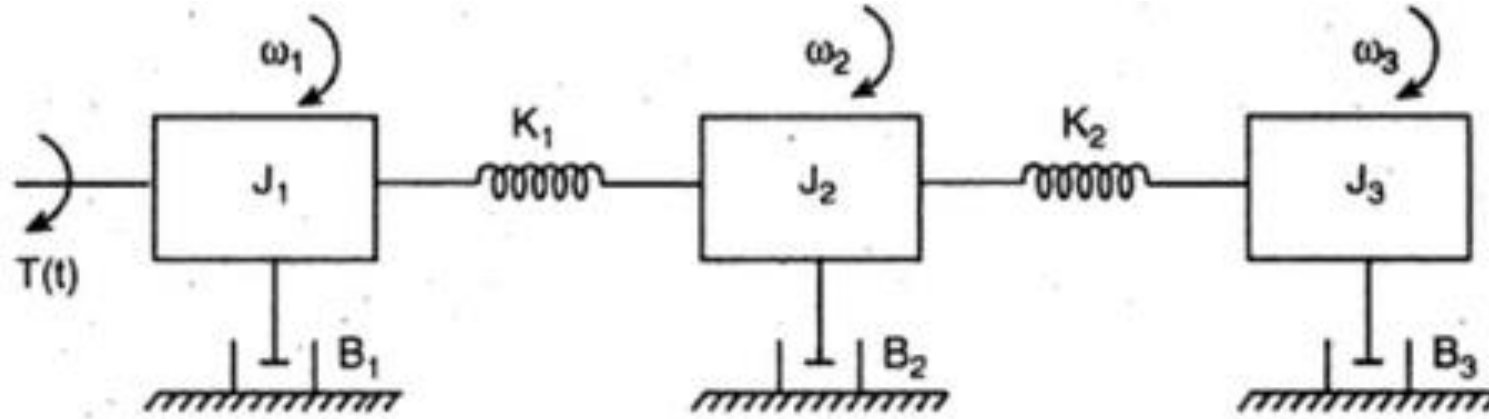


	$T(t)$	$e(t)$	
	$\omega$	$i$	
$J \frac{d\omega}{dt}$	$J$	$L$	$L \frac{di}{dt}$
$B\omega$	$B$	$R$	$iR$
$K \int \omega dt$	$K$	$\frac{1}{C}$	$\frac{1}{C} \int i dt$

$$J_1 \frac{d\omega_1}{dt} + \omega_1 B_1 + K_1 \int (\omega_1 - \omega_2) dt = T(t)$$

$$J_2 \frac{d\omega_2}{dt} + \omega_2 B_2 + K_2 \int (\omega_2 - \omega_3) dt + K_1 \int (\omega_2 - \omega_1) dt = 0$$
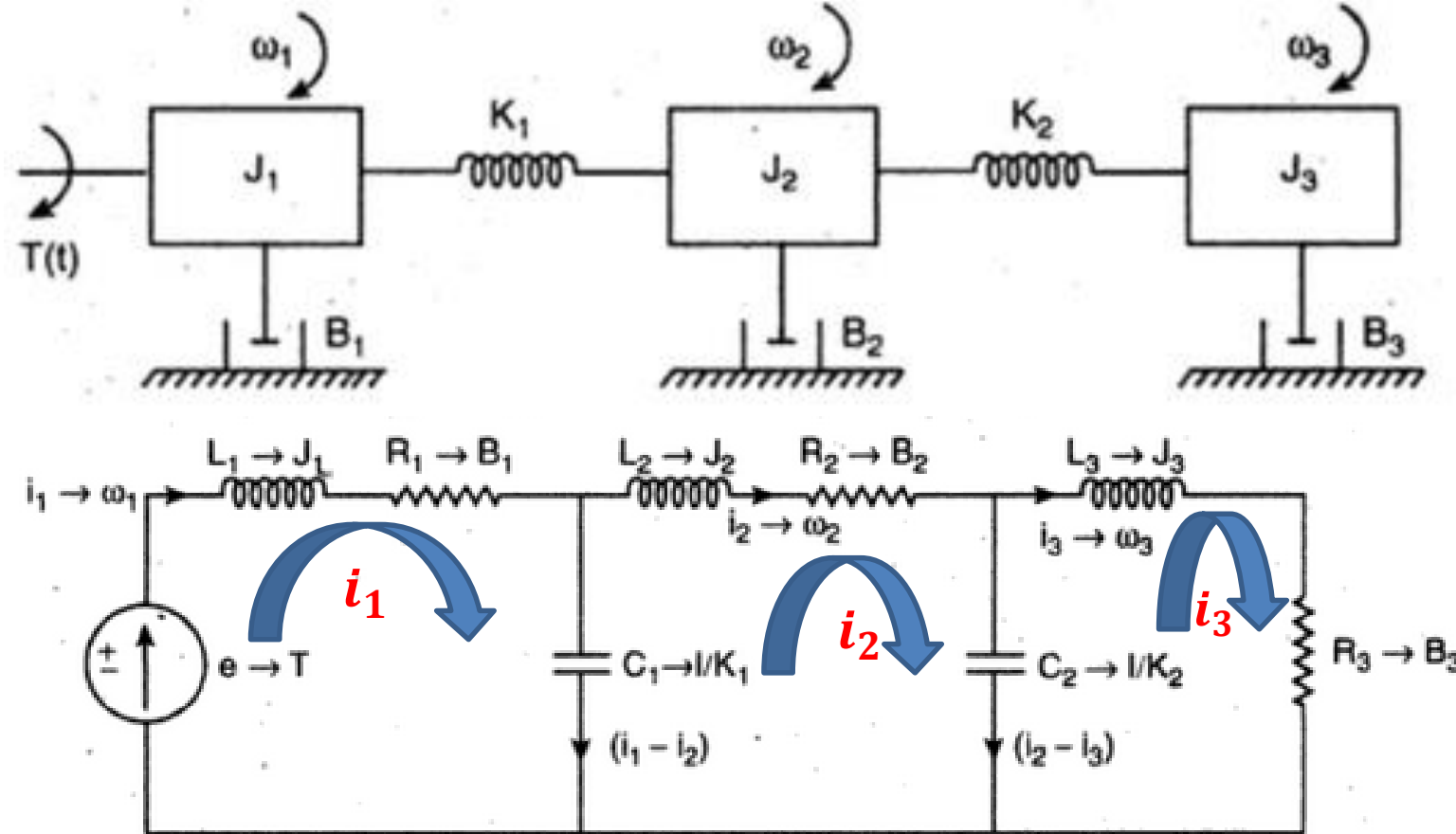
$$J_3 \frac{d\omega_3}{dt} + \omega_3 B_3 + K_2 \int (\omega_3 - \omega_2) dt = 0$$





## TORQUE VOLTAGE ANALOGY

	$T(t)$	$e(t)$	
	$\omega$	$i$	
$J \frac{d\omega}{dt}$	$J$	$L$	$L \frac{di}{dt}$
$B\omega$	$B$	$R$	$iR$
$K \int \omega dt$	$K$	$\frac{1}{C}$	$\frac{1}{C} \int i dt$

$$L_1 \frac{di_1}{dt} + i_1 R_1 + \frac{1}{C_1} \int (i_1 - i_2) dt = e(t)$$

$$L_2 \frac{di_2}{dt} + i_2 R_2 + \frac{1}{C_2} \int (i_2 - i_3) dt + \frac{1}{C_1} \int (i_2 - i_1) dt = 0$$

$$L_3 \frac{di_3}{dt} + i_3 R_3 + \frac{1}{C_3} \int (i_3 - i_2) dt = 0$$

$$J_1 \frac{d\omega_1}{dt} + \omega_1 B_1 + K_1 \int (\omega_1 - \omega_2) dt = T(t)$$

$$J_2 \frac{d\omega_2}{dt} + \omega_2 B_2 + K_2 \int (\omega_2 - \omega_3) dt + K_1 \int (\omega_2 - \omega_1) dt = 0$$


$$J_3 \frac{d\omega_3}{dt} + \omega_3 B_3 + K_2 \int (\omega_3 - \omega_2) dt = 0$$

# TORQUE CURRENT ANALOGY

**MECHANICAL SYSTEM:**     Input – Torque  
                                         Output – Angular Velocity


**ELECTRICAL SYSTEM:**     Input – Current source  
                                         Output – Voltage across the element

**Moment of inertia of Mass**

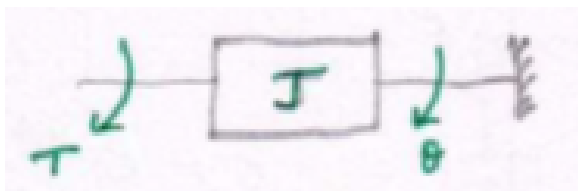


$$T(t) = J \frac{d^2\theta}{dt^2} = J \frac{d\omega}{dt}$$

**Dash pot**

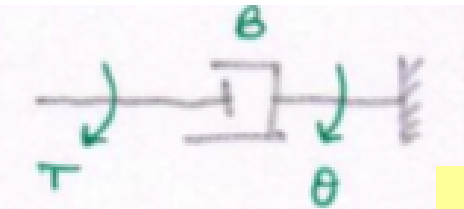

$$T(t) = B \frac{d\theta}{dt} = B\omega$$


**Spring**

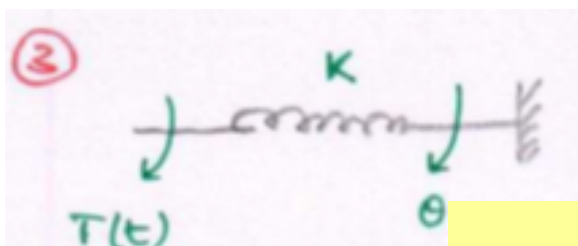

$$T(t) = K\theta = K \int \omega dt$$


	$T(t)$	$i(t)$	
	$\omega$	$e$	
$J \frac{d\omega}{dt}$	$J$	$C$	$C \frac{de}{dt}$
$B\omega$	$B$	$\frac{1}{R}$	$\frac{e}{R}$
$K \int \omega dt$	$K$	$\frac{1}{L}$	$\frac{1}{L} \int e dt$

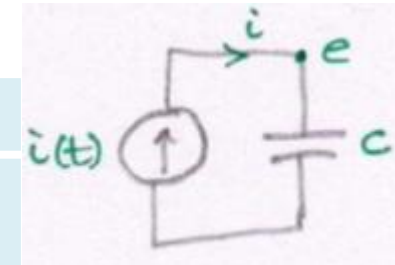$J$  – Polar Moment of Inertia  
 $\theta$  – Angular displacement  
 $\omega$  – Angular velocity




**Capacitance**

$$i(t) = C \frac{de}{dt}$$

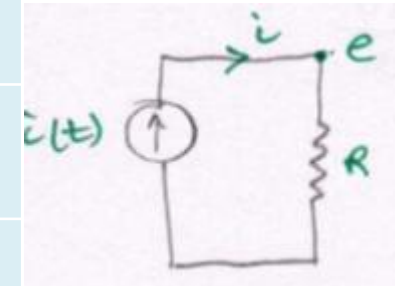

**Resistance**

$$i(t) = \frac{e}{R}$$

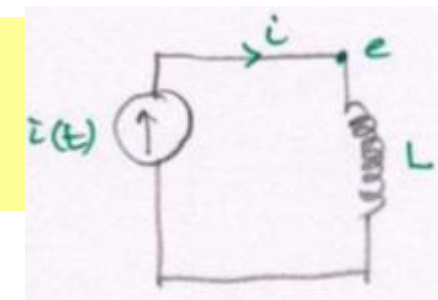

**Inductance**

$$i(t) = \frac{1}{L} \int e dt$$

# TORQUE CURRENT ANALOGY

## MECHANICAL SYSTEM

- Input – Torque
- Output – Angular velocity


## ELECTRICAL SYSTEM

- Input – current source
- Output – voltage across the element

	$T(t)$	$i(t)$	
	$\omega$	$e$	
$J \frac{d\omega}{dt}$	$J$	$C$	$C \frac{de}{dt}$
$B\omega$	$B$	$\frac{1}{R}$	$\frac{e}{R}$
$K \int \omega dt$	$K$	$\frac{1}{L}$	$\frac{1}{L} \int e dt$

- In mechanical systems, elements in parallel have same torque. Similarly, in electrical systems, parallel systems will have same voltage.
- Each mass in the mechanical system corresponds to a node in a electrical system.
- Number of nodes in the electrical system is equal to the number of masses in the mechanical system
- The element connected between two masses in mechanical system is represented by common element between two nodes in electrical system.

# TORQUE CURRENT ANALOGY

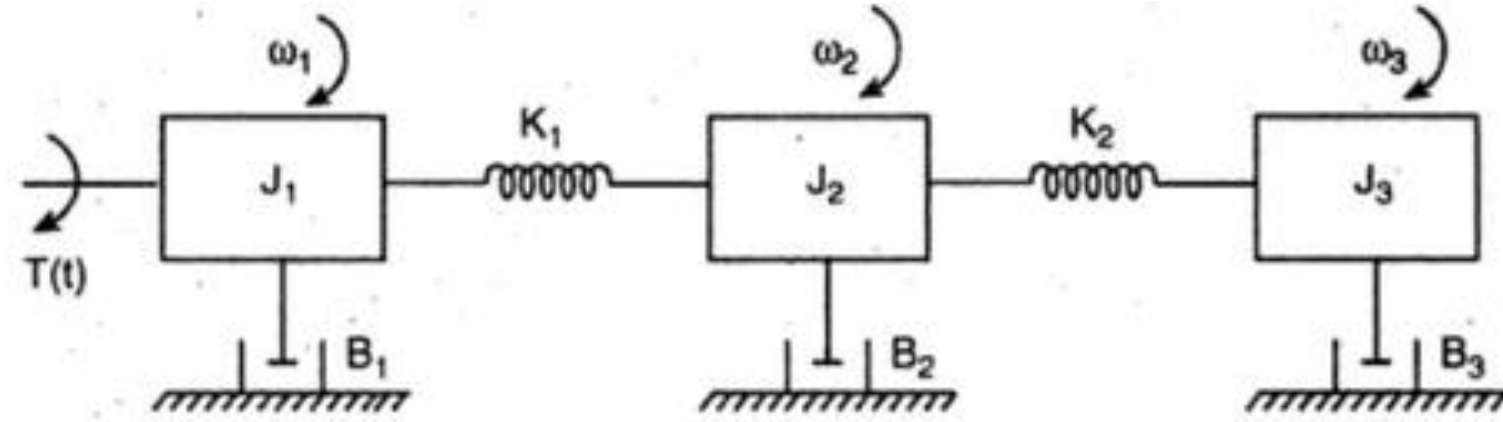


	$T(t)$	$i(t)$	
	$\omega$	$e$	
$J \frac{d\omega}{dt}$	$J$	$C$	$C \frac{de}{dt}$
$B\omega$	$B$	$\frac{1}{R}$	$\frac{e}{R}$
$K \int \omega dt$	$K$	$\frac{1}{L}$	$\frac{1}{L} \int e dt$

$$J_1 \frac{d\omega_1}{dt} + \omega_1 B_1 + K_1 \int (\omega_1 - \omega_2) dt = T(t)$$

$$J_2 \frac{d\omega_2}{dt} + \omega_2 B_2 + K_2 \int (\omega_2 - \omega_3) dt + K_1 \int (\omega_2 - \omega_1) dt = 0$$
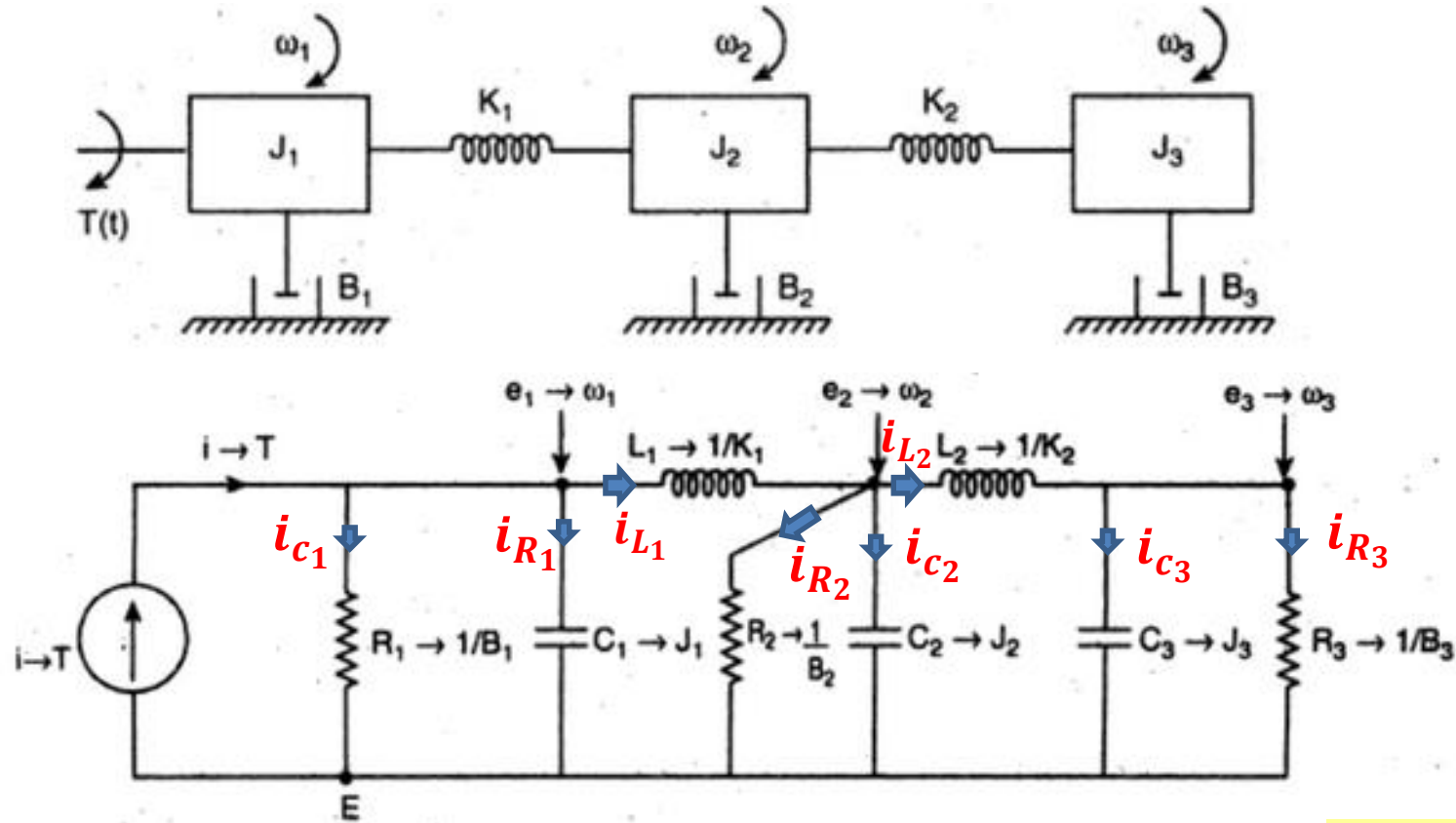
$$J_3 \frac{d\omega_3}{dt} + \omega_3 B_3 + K_2 \int (\omega_3 - \omega_2) dt = 0$$



## TORQUE CURRENT ANALOGY

	$T(t)$	$i(t)$	
	$\omega$	$e$	
$J \frac{d\omega}{dt}$	$J$	$C$	$C \frac{de}{dt}$
$B\omega$	$B$	$\frac{1}{R}$	$\frac{e}{R}$
$K \int \omega dt$	$K$	$\frac{1}{L}$	$\frac{1}{L} \int edt$

Node  $e_1$ ,  $i(t) = i_{c_1} + i_{R_1} + i_{L_1}$

$$C_1 \frac{de_1}{dt} + \frac{e_1}{R_1} + \frac{1}{L_1} \int (e_1 - e_2) dt = i(t)$$

Node  $e_2$ ,  $i_{L_1} = i_{c_2} + i_{R_2} + i_{L_2}$


$$\frac{1}{L_1} \int (e_1 - e_2) dt = C_2 \frac{de_2}{dt} + \frac{e_2}{R_2} + \frac{1}{L_2} \int (e_2 - e_3) dt$$

$$C_2 \frac{de_2}{dt} + \frac{e_2}{R_2} + \frac{1}{L_2} \int (e_2 - e_3) dt + \frac{1}{L_1} \int (e_2 - e_1) dt = 0$$

Node  $e_3$ ,  $i_{L_2} = i_{c_3} + i_{R_3}$

$$\frac{1}{L_2} \int (e_2 - e_3) dt = C_3 \frac{de_3}{dt} + \frac{e_3}{R_3}$$
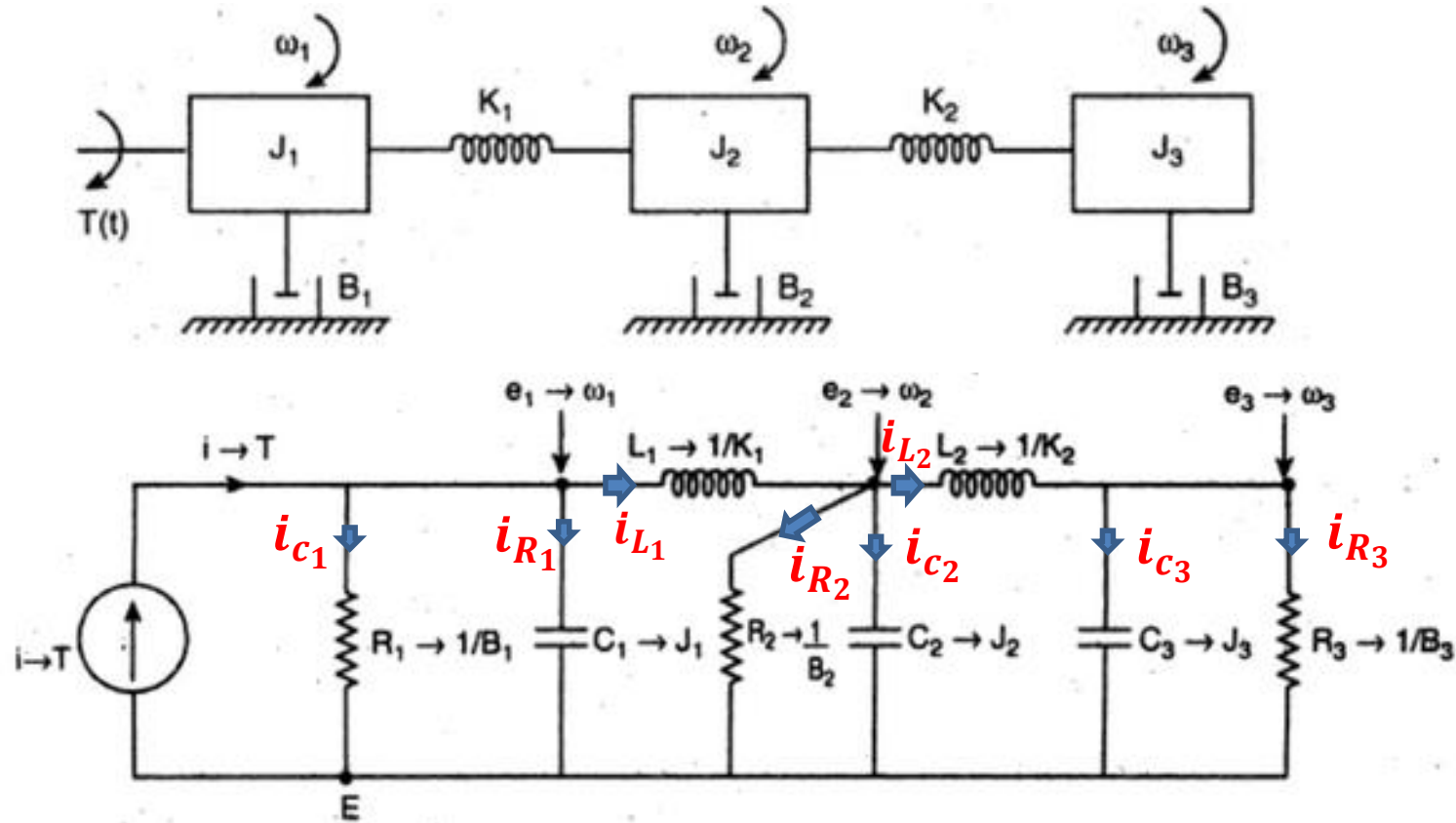
$$C_3 \frac{de_3}{dt} + \frac{e_3}{R_3} + \frac{1}{L_2} \int (e_3 - e_2) dt = 0$$



## TORQUE CURRENT ANALOGY

	$T(t)$	$i(t)$	
	$\omega$	$e$	
$J \frac{d\omega}{dt}$	$J$	$C$	$C \frac{de}{dt}$
$B\omega$	$B$	$\frac{1}{R}$	$\frac{e}{R}$
$K \int \omega dt$	$K$	$\frac{1}{L}$	$\frac{1}{L} \int e dt$

$$C_1 \frac{de_1}{dt} + \frac{e_1}{R_1} + \frac{1}{L_1} \int (e_1 - e_2) dt = i(t)$$

$$C_2 \frac{de_2}{dt} + \frac{e_2}{R_2} + \frac{1}{L_2} \int (e_2 - e_3) dt + \frac{1}{L_1} \int (e_2 - e_1) dt = 0$$

$$C_3 \frac{de_3}{dt} + \frac{e_3}{R_3} + \frac{1}{L_2} \int (e_3 - e_2) dt = 0$$

$$J_1 \frac{d\omega_1}{dt} + \omega_1 B_1 + K_1 \int (\omega_1 - \omega_2) dt = T(t)$$

$$J_2 \frac{d\omega_2}{dt} + \omega_2 B_2 + K_2 \int (\omega_2 - \omega_3) dt + K_1 \int (\omega_2 - \omega_1) dt = 0$$

$$J_3 \frac{d\omega_3}{dt} + \omega_3 B_3 + K_2 \int (\omega_3 - \omega_2) dt = 0$$